

# HOW TO SOLVE SMITH CHART CERTAIN PROBLEMS SPECIAL CASES OF SMITH CHART

**AHMAD BILAL**

**SWEDISHCHAP.WEEBLY.COM**

## Q1 : Calculate Reflection Constant on Smith chart

1. Get normalized impedance
2. Plot the impedance
3. Draw a line from origin to the outside of smith chart, crossing impedance.
4. Using a scale or compass note down the magnitude and angle of reflection co-efficient

## Practice Question

A transmission line has a reflection coefficient of 0.6 at an angle of 45 degree. Represent the same graphically on smith chart

## Q2: Find z at the distance "l" from the load

1. Get normalized impedance
2. Plot the impedance
3. Get length in term of Impedance

$$2\pi = 2\beta l = 2 \cdot \frac{2\pi}{\lambda} \cdot l$$

4. Move clock wise or anti clock wise l times and mark new impedance

## Practice Question

## INCLUDES

How To Plot Smith


Chart and Practice

exercises

Q1: Show graphically Transmission co-efficient on smith chart with magnitude of 1.55 and angle of 45

Q2: A line with 50 ohm impedance has a Zl of  $50+j50$ . Calculate the angle of transmission and reflection coefficient. What will be the change in angle of transmission and reflection coefficient, if the resistance is increased 30 times

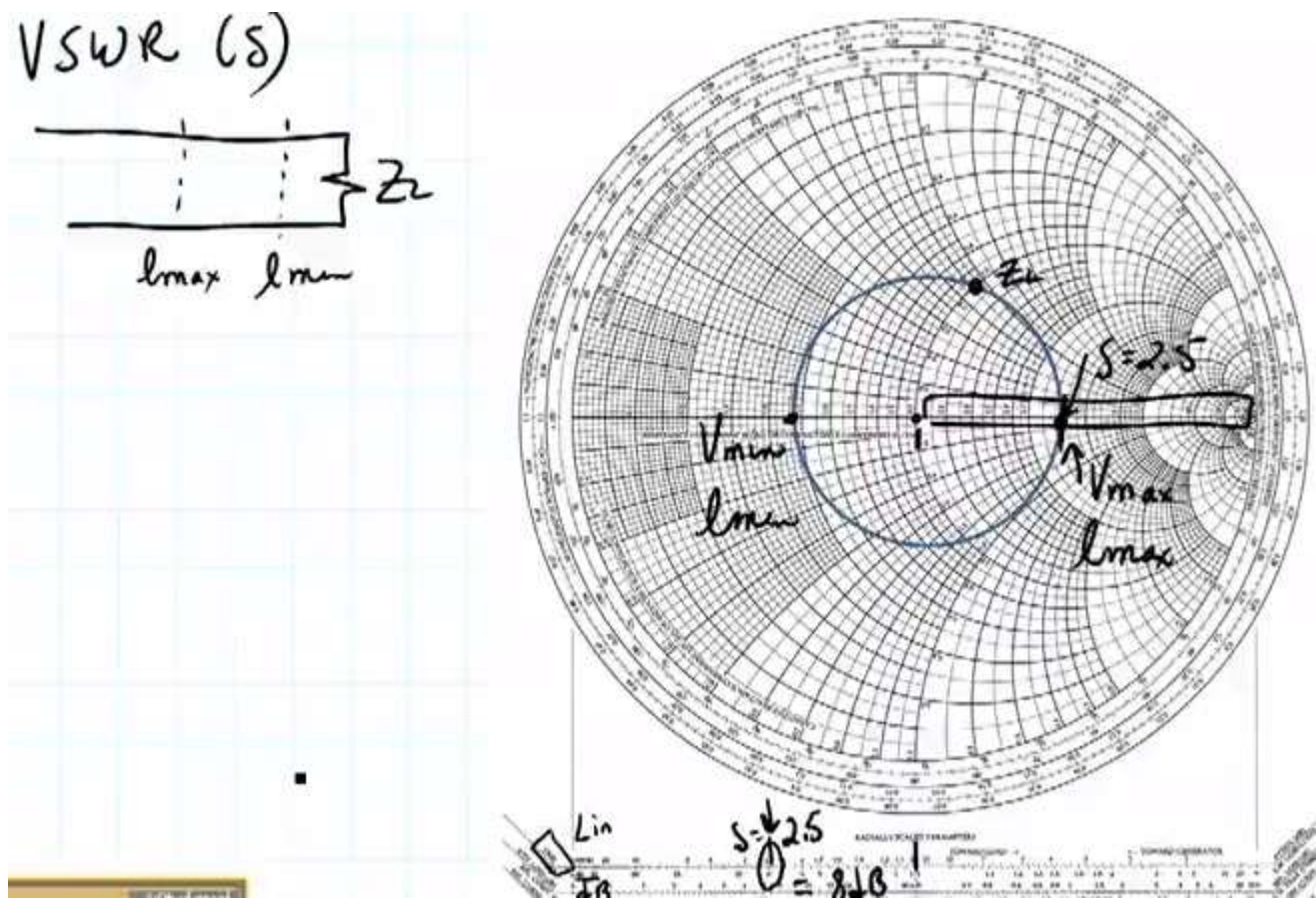**Q2: Find VSWR and Load Maximum and Minimum**




Practice Question

Q1: Calculate the new impedance for a given  $Z_L = 100 + j50$ , with a impedance of 50 ohm when we have moved towards the generator from load by length of  $.0.2 \lambda$ . Also calculate VSWR and reflection co-efficient


Q2.  $Z_L$  and  $Z_{in}$  are separated by a distance of  $0.2 \lambda$ . If  $Z_L$  has impedance of  $50 + 100j$ . What will be the Admittance and Input Load?

# PRACTICE WORK SHEET

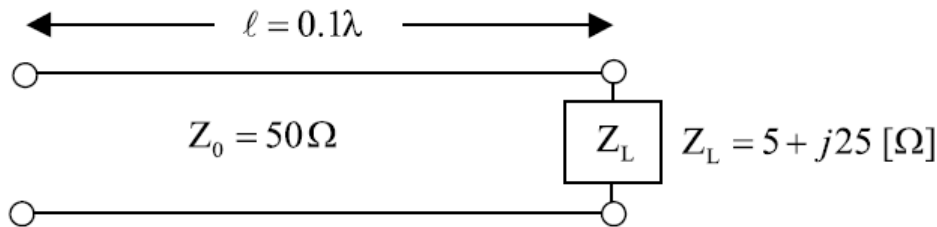

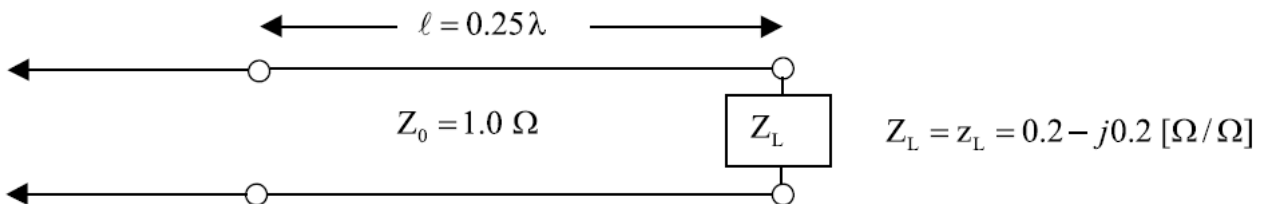1. The  $0.1\lambda$  length line shown has a characteristic impedance of  $50\Omega$  and is terminated with a load impedance of  $Z_L = 5 + j25\Omega$ .


- Locate  $Z_L$
- What is the impedance at  $\ell = 0.1 \lambda$ ?
- Calculate VSWR and Reflection coefficient
- What is Reflection Co-efficient at  $\ell = 0.1 \lambda$  from the load



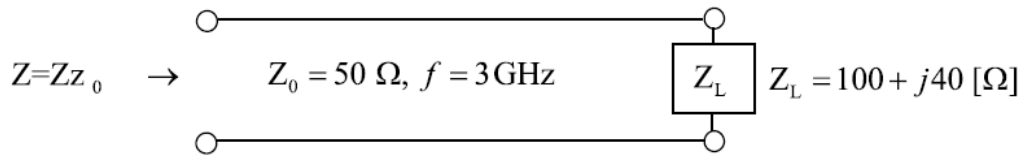2. A transmission line has  $Z_0 = 1.0$ ,  $Z_L = z_L = 0.2 - j0.2\Omega$ .

- What is  $Z$  at  $\ell$  of  $0.25 \lambda$ ?

- Calculate VSWR ,
- Find Maxima and minima




3. The air-filled two-wire line has a characteristic impedance of  $50 \Omega$  and is operated at  $f = 3 \text{ GHz}$ . The load is  $Z_L = 100 + j40 \Omega$ .

- Find  $Z_L$
- Find Impedance at the distance of  $2.5 \text{ cm}$  from the load
- VSWR and angle of transmission

Q4: Suppose we have a transmission line with a characteristic impedance of  $50 \text{ ohms}$  and an electrical length of  $0.3\lambda$ . Also, suppose we terminate this line with an impedance having a resistive component of  $25 \text{ ohms}$  and an inductive reactance of  $25 \text{ ohms}$ . What is the input impedance to the line?

Q5: A loss free transmission line of characteristic impedance  $50 \Omega$  is terminated with a real impedance of  $30 + j100 \Omega$ . If the line is lengthened by  $0.093 \lambda$ , what is the value of the new termination required to ensure that the impedance seen by the generator is unchanged?


Q6 : Solve

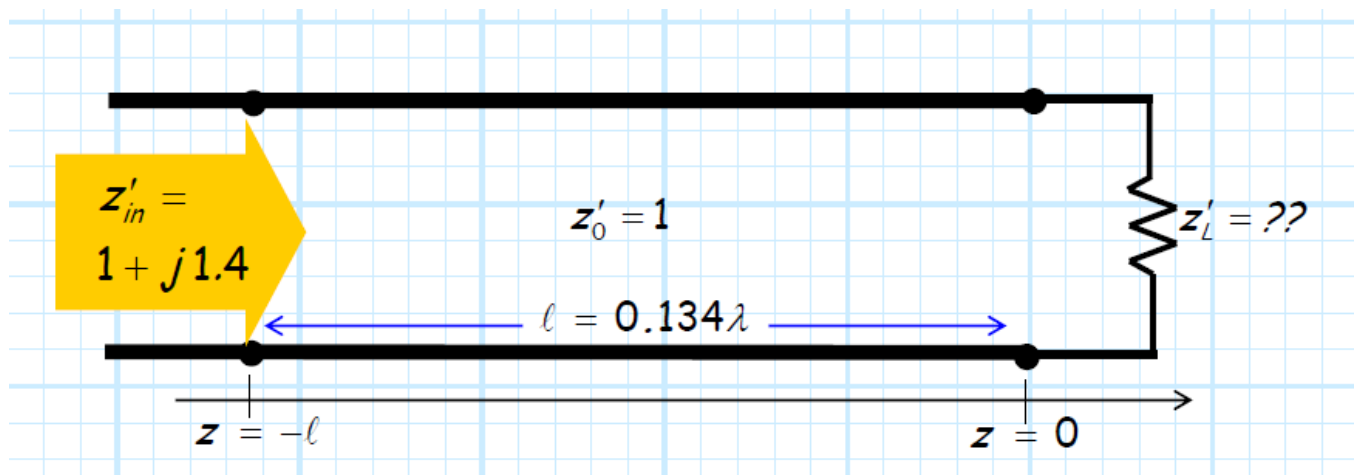

Q7 : A load terminating at transmission line has a normalized impedance  $z_L' = 2.0 + j 2.0$ . What should the length  $l$  of transmission line be in order for its input impedance to be:

- purely real
- have a real (resistive) part equal to one

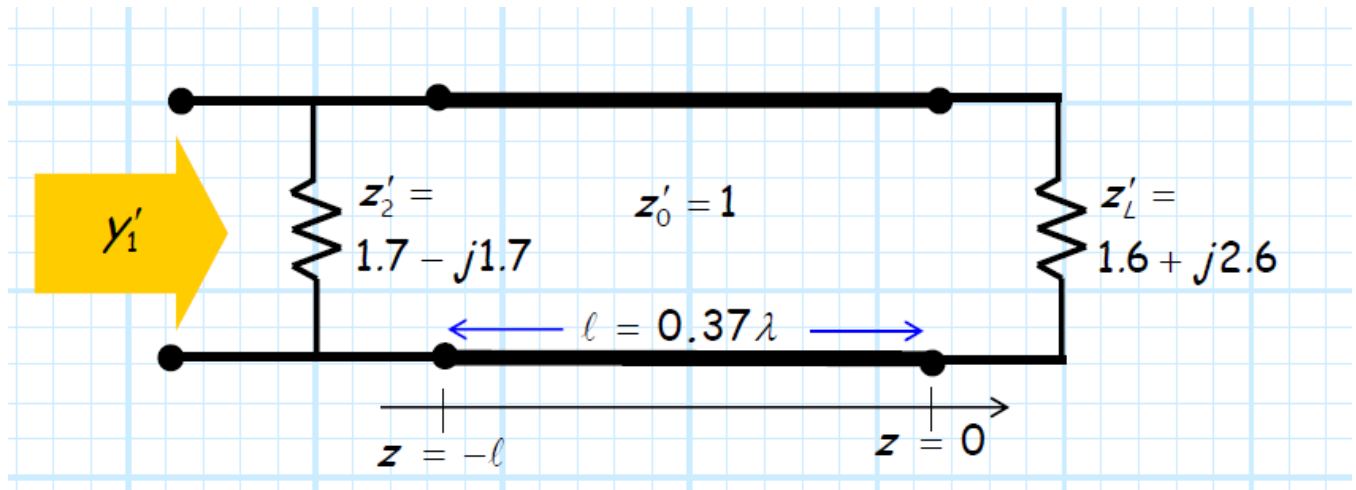Q8 determine the normalized admittance of the network below:



### Practice Questions: Pozar Uncle

2.8

2.9

2.12

2.17

2.18

2.19

2.20

2.21

### Practice Questions : Uncle Peter

Example 3.6

**Example 3.7**

**Example 3.8**