



Microwave Engineering

Ahmad Bilal
Electronics
5th


EID MUBARIK

EID MUBARIK AND CONGRATS TO ALL PEOPLE WHO PASSED SUPPLY

AND CONGRATS TO ALL PEOPLE WHO PASSED SUPPLY

Incident, Reflected, and Absorbed Power

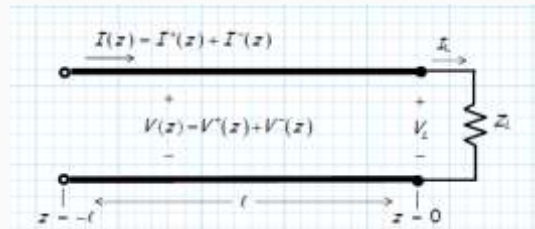
We have discovered that **two waves propagate** along a transmission line, one in each direction ($V^+(z)$ and $V^-(z)$)



How much power flows along a transmission line, and where does that power go?

We can answer that question by determining the power **absorbed** by the **load**!

Recall Signal And System

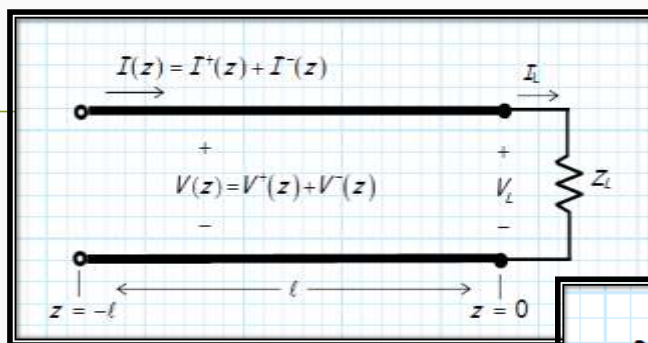

$$P_{abs} = \frac{1}{2} \text{Re}\{V_L I_L^*\}$$

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} \\
 &= \frac{1}{2} \operatorname{Re}\{V(z=0)I(z=0)^*\} \\
 &= \frac{1}{2 Z_0} \operatorname{Re}\left\{\left(V_0^+ [e^{-j\beta 0} + \Gamma_0 e^{+j\beta 0}]\right) \left(V_0^+ [e^{-j\beta 0} - \Gamma_0 e^{+j\beta 0}]\right)^*\right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} \operatorname{Re}\{1 - (\Gamma_0^* - \Gamma_0) - |\Gamma_0|^2\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_0|^2)
 \end{aligned}$$

Can we Solve
it More ?



Solving Equation

- Sure We can

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_0|^2) = \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^+ \Gamma_0|^2}{2 Z_0} = \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^-|^2}{2 Z_0}$$

Yeh Kahan
say agaya?



Playing With Equation

Divide The Equation in two parts

$$P_{abs} = P_{inc} + P_{refl}$$

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} - \frac{|V_0^-|^2}{2Z_0}$$

P_{inc}

We say that this wave is **incident** on the load:

$$P_{inc} = P_+ = \frac{|V_0^+|^2}{2Z_0}$$

P_{ref}

$$P_{ref} = P_- = \frac{|V_0^-|^2}{2Z_0} = \frac{|\Gamma_L V_0^+|^2}{2Z_0}$$

Shabash Bacha Log ??

$$P_{ref} = P_- = \frac{|V_0^-|^2}{2Z_0} = \frac{|\Gamma_L V_0^+|^2}{2Z_0} = |\Gamma_L|^2 \frac{|V_0^+|^2}{2Z_0} = |\Gamma_L|^2 P_{inc}$$

Concluding : The Boring Power




$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} - \frac{|V_0^-|^2}{2Z_0} = P_{inc} - P_{ref}$$

ig, we find:

$$P_{inc} = P_{abs} + P_{ref}$$

Summing it all...

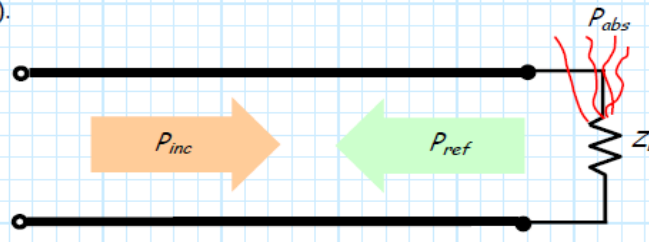It says that power flowing **toward** the load (P_{inc}) is either **absorbed** by the load (P_{abs}) or **reflected** back from the load (P_{ref}).



When Reflection Coefficient is 1

- $|\Gamma_L|^2 = 1$


For this case, we find that the load absorbs **no power!**

$$P_{abs} = P_{inc} (1 - |\Gamma_L|^2) = P_{inc} (1 - 1) = 0$$

Likewise, we find that the reflected power is **equal** to the incident:

$$P_{ref} = |\Gamma_L|^2 P_{inc} = (1) P_{inc} = P_{inc}$$

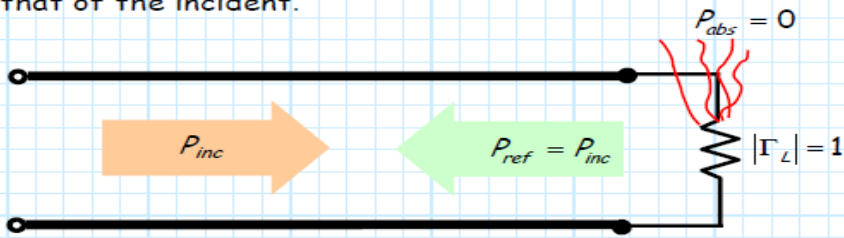In this case, **no power** is absorbed by the load. **All** of the incident power is **reflected**, so that the reflected power is **equal** to that of the incident.



When Reflection : Coefficient is Zero

2. $|\Gamma_L| = 0$

For this case, we find that there is **no reflected power!**

$$P_{ref} = |\Gamma_L|^2 P_{inc} = (0) P_{inc} = 0$$

Likewise, we find that the absorbed power is **equal** to the incident:


$$P_{abs} = P_{inc} (1 - |\Gamma_L|^2) = P_{inc} (1 - 0) = P_{inc}$$

Note these two results are completely **consistent**—by conservation of energy, if one is true the other **must** also be:

Questions

- What will Happen if reflection coefficient is greater than 1
- Can Reflection Coefficient can be greater than 1

Can I calculate Z_{in} ?

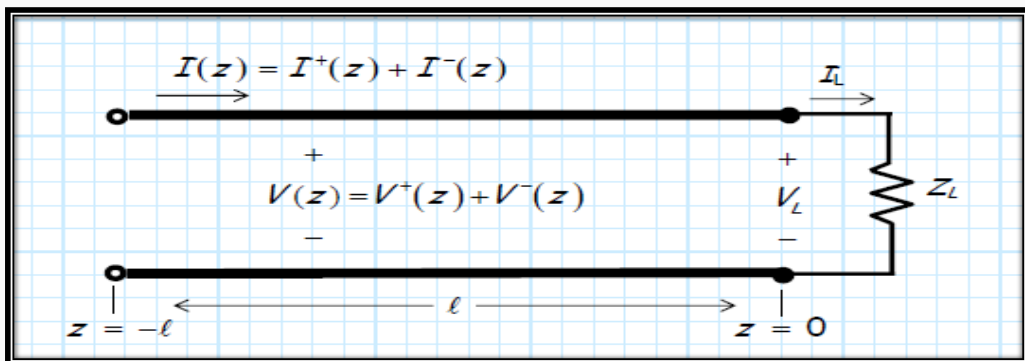

Calculating Z_{in}

- We Know any Impedance is ratio of Voltage and Current so for Z_{in}

$$Z_{in} = Z(z = -\ell) = \frac{V(z = -\ell)}{I(z = -\ell)}$$

Step 2: Determining Voltage and Current

$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_0 e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_0 e^{-j\beta\ell}]$$

Therefore:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left(\frac{e^{+j\beta\ell} + \Gamma_0 e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_0 e^{-j\beta\ell}} \right)$$

Step 3 : Calculating Impedance at Any Point

- Recall ...



For Loss Less transmission Line , Propagation
factor is

Putting Values and Finalizing

$$Z_{in} = Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right)$$

$$= Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right)$$

Finalizing Values

Resource : Ahsan's
Brain Xray

Special Cases

Now let's look at the Z_{in} for some important **load impedances** and **line lengths**.

→ You should commit these results to **memory!**



Case 1

$$1. \ell = \lambda/2$$



If the length of the transmission line is exactly **one-half wavelength** ($\ell = \lambda/2$), we find that:

$$\beta\ell = \frac{2\pi}{\lambda} \frac{\lambda}{2} = \pi$$

meaning that:

$$\cos \beta\ell = \cos \pi = -1 \quad \text{and} \quad \sin \beta\ell = \sin \pi = 0$$


Case 1... Cont

and therefore:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta\ell + j Z_0 \sin \beta\ell}{Z_0 \cos \beta\ell + j Z_L \sin \beta\ell} \right) \\ &= Z_0 \left(\frac{Z_L (-1) + j Z_0 (0)}{Z_0 (-1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

In other words, if the transmission line is precisely **one-half wavelength** long, the **input impedance** is equal to the **load impedance**, regardless of Z_0 or β .

$$Z_{in} = Z_L$$

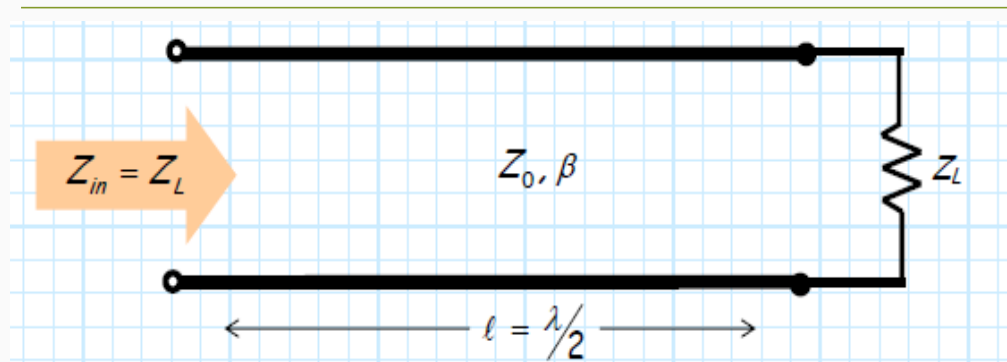

Case 2

2. $l = \lambda/4$

If the length of the transmission line is exactly **one-quarter** wavelength ($l = \lambda/4$), we find that:

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

meaning that:

$$\cos \beta l = \cos \pi/2 = 0 \quad \text{and} \quad \sin \beta l = \sin \pi/2 = 1$$

Case 2 .. Cont

and therefore:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_L (0) + j Z_0 (1)}{Z_0 (0) + j Z_L (1)} \right) \\ &= \frac{(Z_0)^2}{Z_L} \end{aligned}$$


In other words, if the transmission line is precisely **one-quarter wavelength** long, the **input impedance** is **inversely** proportional to the **load impedance**.

Case III $Z_L = Z_0$

If the load is **numerically equal** to the characteristic impedance of the transmission line (a real value), we find that the input impedance becomes:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_0 \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_0 \sin \beta l} \right) \\ &= Z_0 \end{aligned}$$

In other words, if the load impedance is equal to the transmission line **characteristic impedance**, the **input impedance** will be likewise be equal to Z_0 regardless of the transmission line length ℓ .

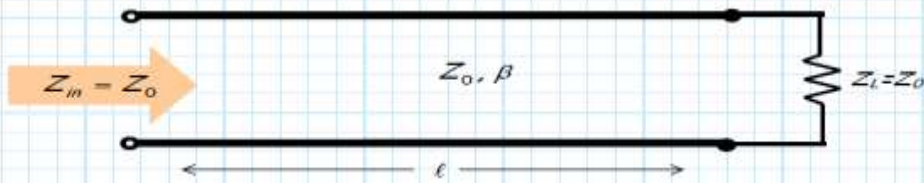

Case 4

4. $Z_L = jX_L$


If the load is **purely reactive** (i.e., the resistive component is zero), the input impedance is:

Case 4 ... Cont

$$\begin{aligned}
 Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\
 &= Z_0 \left(\frac{j X_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j^2 X_L \sin \beta l} \right) \\
 &= j Z_0 \left(\frac{X_L \cos \beta l + Z_0 \sin \beta l}{Z_0 \cos \beta l - X_L \sin \beta l} \right)
 \end{aligned}$$

Case 4 .. Cont

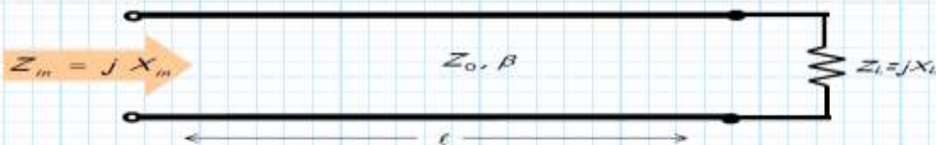In other words, if the load is purely reactive, then the input impedance will **likewise** be purely reactive, **regardless** of the line length ℓ .



Note that the **opposite is not true**: even if the load is **purely resistive** ($Z_L = R$), the input impedance will be **complex** (both resistive and reactive components).

Case 5

5. $\ell \ll \lambda$

If the transmission line is **electrically small**—its length ℓ is small with respect to signal wavelength λ —we find that:

$$\beta\ell = \frac{2\pi}{\lambda}\ell = 2\pi\frac{\ell}{\lambda} \approx 0$$

and thus:

$$\cos \beta\ell = \cos 0 = 1 \quad \text{and} \quad \sin \beta\ell = \sin 0 = 0$$

Case 5 Contd


so that the input impedance is:

$$\begin{aligned} Z_m &= Z_0 \left(\frac{Z_L \cos \beta\ell + j Z_0 \sin \beta\ell}{Z_0 \cos \beta\ell + j Z_L \sin \beta\ell} \right) \\ &= Z_0 \left(\frac{Z_L (1) + j Z_L (0)}{Z_0 (1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

In other words, if the transmission line length is much smaller than a wavelength, the **input impedance** Z_m will **always** be equal to the **load impedance** Z_L .



Calculate Z_{in} !!!!

Consider the following circuit:

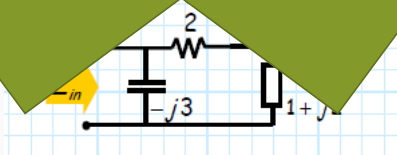


So now Calculate

Consider the following circuit:

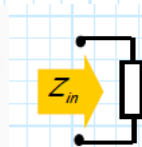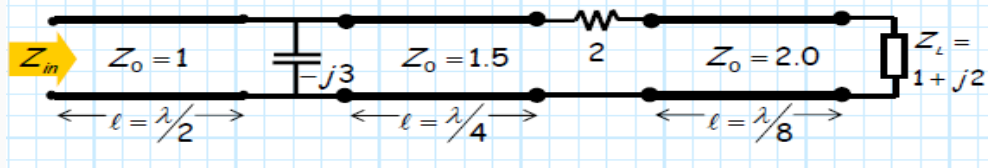

Step 1

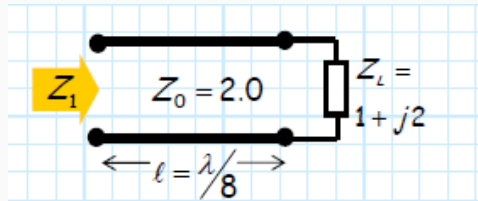


we find that Z_1 is :


$$\begin{aligned}
 Z_1 &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\
 &= 2 \left(\frac{(1 + j2) \cos(\pi/4) + j 2 \sin(\pi/4)}{2 \cos(\pi/4) + j(1 + j2) \sin(\pi/4)} \right) \\
 &= 2 \left(\frac{1 + j4}{j} \right) \\
 &= 8 - j2
 \end{aligned}$$

Step 2: Redraw Circuit

Consider the following circuit:

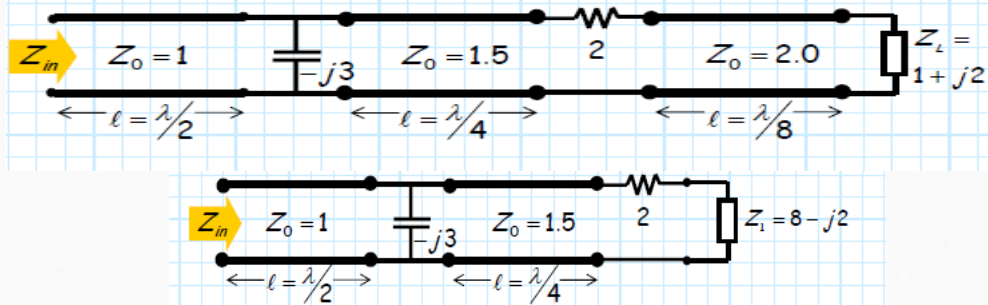


Step 3

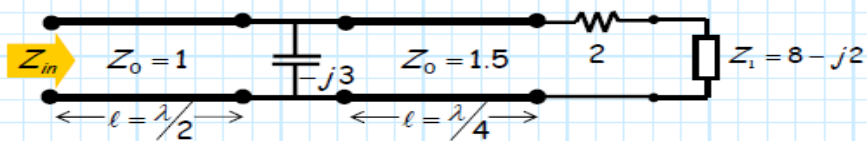


Note the resistor is in **series** with impedance Z_1 . We can **combine** these two into one impedance defined as Z_2 :
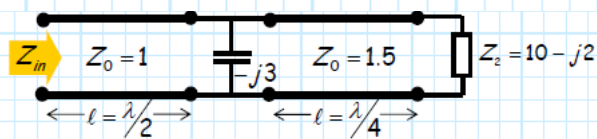
$$Z_2 = 2 + Z_1 = 2 + (8 - j2) = 10 - j2$$



Step 4

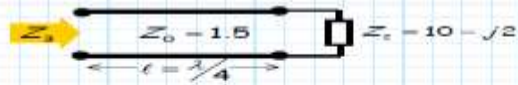


Note that this transmission line is a **quarter wavelength** ($l = \lambda/4$). This is one of the **special cases** we considered earlier! The input impedance Z_{in} is:


$$\begin{aligned} Z_{in} &= \frac{Z_0 Z_L + Z_0^2}{Z_0 + Z_L} \\ &= \frac{1.5(10 - j2) + 1.5^2}{1.5 + 10 - j2} \\ &= \frac{1.5^2}{10 - j2} \\ &= 0.21 + j0.043 \end{aligned}$$

Step 5

- Redrawing Circuit

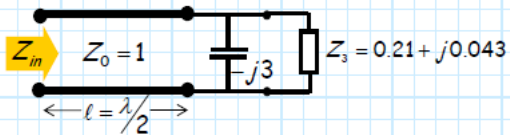

Step 6

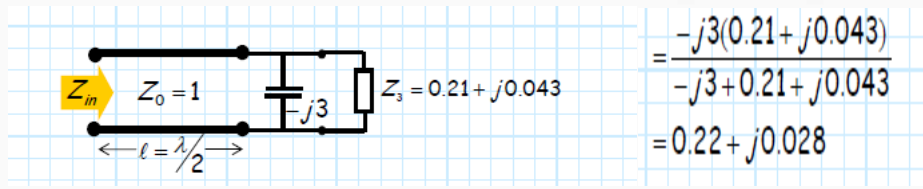

DRAW

