


Sample Paper 1

Derive an expression for Power along Transmission Line. And Discuss Some Special cases of Power with respect to Γ_L

(6)

Q1- B) Find Z_{in}

(6)

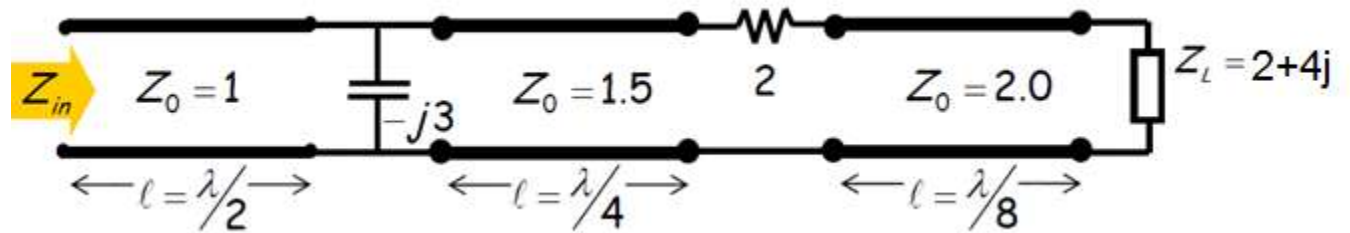


Explain Quarter Wave Transformation. Use lambda by four transformer to match a 300 ohm line to a 75 load , such that there is no SWR and calculate the value of transformer

(3)

For the Following circuit find


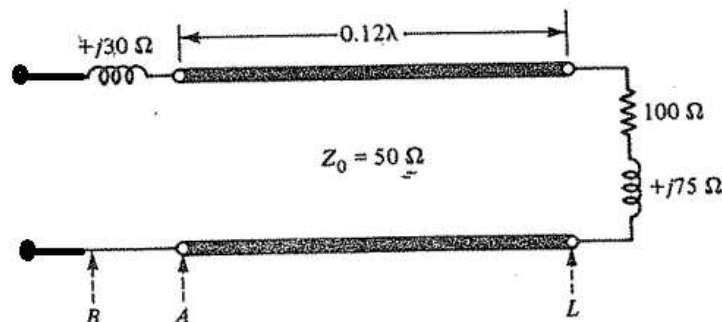
(6)

- The SWR for load
- Reflection Coefficient at the load
- Transmission Coefficient at the load
- Input Impedance
- The distance of the of load to first voltage maxima
- The distance of load to first Minima



Find Two Solutions for each of the following cases for single stub where value of $Z_0=100$ Ohm

(5+5)

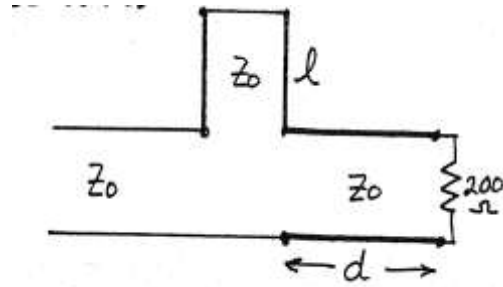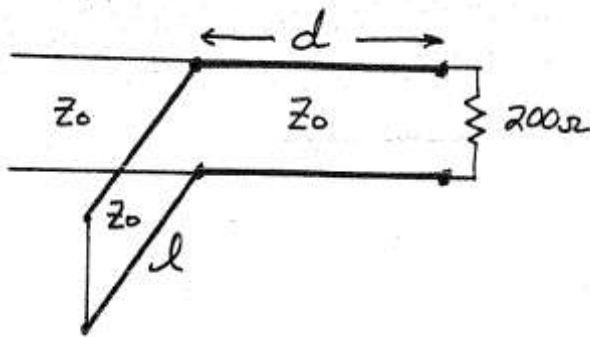

Explain wave Guide in details, and compare them, with transmission Lines. Explain and derive expressions for wave guide while developing TEM and TM_m Modes where $m=1$ (8)

Derive an Expression for Impedance matrix, and create a relation with Admittance Matrix (5)
 A T-pad attenuator is required to reduce the level of an audio signal by 18dB while matching the impedance of the 600Ω network. Calculate the values of the three resistors required. (4)

Draw Diagram of TWT and briefly describe TWT (6)
 Explain Briefly (6)
 a) Flanges
 b) Quarter Wave Transform

Develop an Expression for Transmission Line Input Impedance. Discuss Some Special cases of Input Impedance with respect to load impedance and length of line


(6)
 A 50 Ohm line is terminated in a 75 Ohm resistor, The input terminals are connected to output of a 30 OHM line . Both lines are 0.12 Lambda long (6)

- Find Z_{in} and Z_o at the input of 30 Ohm Line
- Find SWR

For the following Transmission line circuit. Find (6)


- The SWR for load
- Reflection Coefficient at the load
- Transmission Coefficient at the load
- Input Impedance

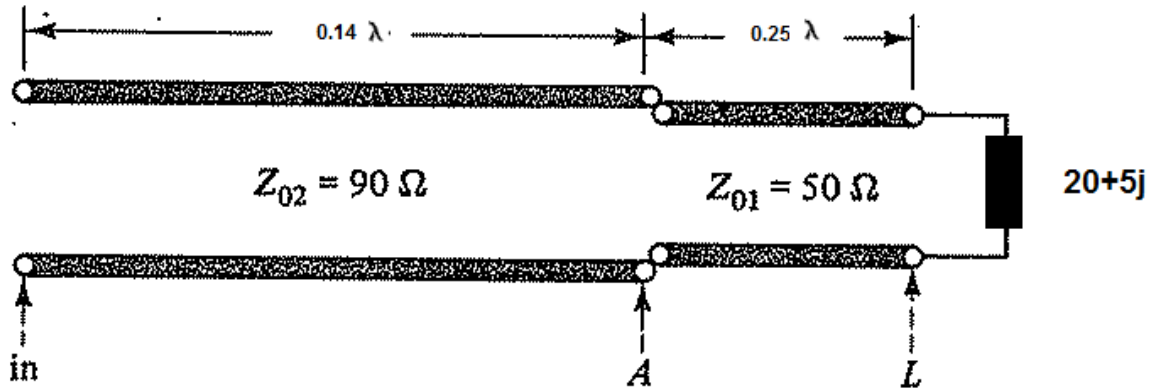- The distance of the of load to first voltage maxima
- The distance of load to first Minima



:Find two possible solutions for each stub , attached to Transmission line for impedance matching purposes

(5+5)

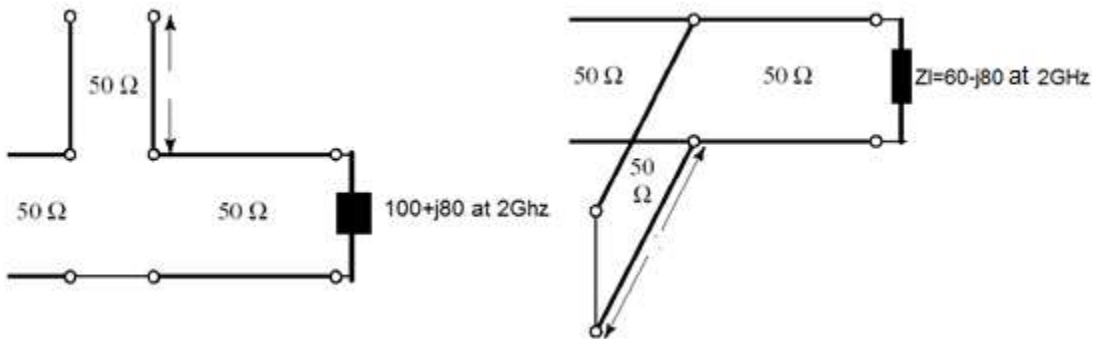


What are different type of Transmission Modes? Explain them (2)

What do you mean by mode, and how it be interpreted graphically (3)

Explain mathematically why does TE₀ do not exist whereas TM₀ exist (6)

Pi-pad attenuator circuit is required to reduce the level of an signal by 10dB while matching the impedance of a 75Ω network. Calculate the values of the three resistors required and Label a Pi pad Attenuator diagram as per the obtained values (4)

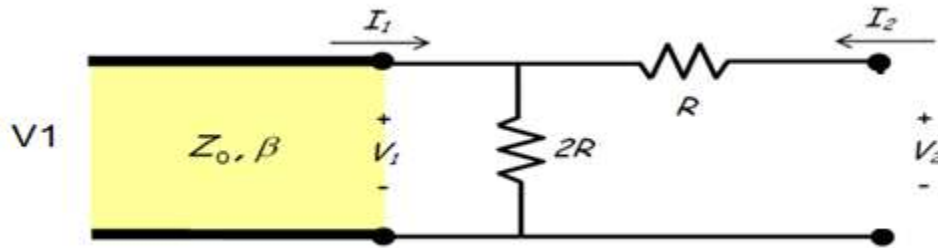Determine type of network represented by following port using admittance matrix (5)



Draw Diagram of Magnetron and briefly describe it

(6) Explain Briefly
(6)

- a) Co-axial Cable
- b) Comparison Table for transmission line and Wave Guides

What are diodes . Explain Gunn diodes, PIN diodes and IMPATT Diodes and Tunnel diode . Explain their working at construction with diagram (12)

What are different method of exciting wave guides. Explain them (8)

What is microstrip line (4)

A 50 Ohm line is terminated in a 75 Ohm resistor, The input terminals are connected to output of a 30 OHM line . Both lines are 0.12 Lambda long. Using Smith chart , find

- The SWR fort load
- Reflection Coefficient at the load
- Transmission Coefficient at the load
- Input Impedance
- The distance of the of load to first voltage maxima
- The distance of load to first Minima

Define different type of networks on the basis of matrixes (4)

Make field patterns for TE and TM mode (8)

Write detailed note on (8 marks each) * This question appeared in in Final term of Islamia university(8 marls Each)

- **Microwave Attenuator**
- **Microwave Mixers**
- **Microwave Circulator**
- **Microwave Isolators**
- **Microwave Detectors**

Class : I just received these above topics and I am working o their notes. They will be availbale by 9 : 00 PM on website Mea while you prepare rest.